Student: Frasineanu Claudia Andreea

Group: CEN 3.2A Project number: 31

PIC24 Documentation

In the table below are the specific instructions corresponding to my project's number:

Non-jump Instructions	Flags	Jump Instructions
LSR Wb, #lit4, Wnd	OV	BRA OV, Expr
ZE Ws, Wnd	С	BRA C, Expr
BTST.Z Ws, #bit4	N	BRA N, Expr
INC Ws, Wd	Z	BRA Z, Expr

The microprocessor is composed of a total of 9 individual elements, each having an important and crucial role. Starting from the upper leftmost element, we have the following blocks:


I. PC Update

This block is responsible for computing the new value of the *Program Counter (PC)*. Depending on the type of the instruction, the new value of the PC will either be:

- PC + 2, for a normal instruction;
- PC + 2 + offset*2, for a branch instruction.

In the last case, a left shift is performed on the offset before it is added. The offset can be parsed from bits $15 \rightarrow 0$, but we can also use just the last 5 bits.

 It should be noted that the new value of the PC



is only an intermediar value, and will not be attributed to the PC through this block.

II. **Program Counter**

This is the block responsible for attributing the newly determined value of the PC. The block takes the value computed in the previous block (PC Update) and attributes it to the PC.

As a remark, this operation will only be performed on a rising edge of the Clock (or when the signal changes from 0 to 1).



III. ROM32x24

This block represents the memory of the microprocessor. It contains 32 words, each word having 24 bits.

PC(5:1) Addr(4:0) Data(23:0)

Using the first 5 bits of the *PC*, the corresponding word will be chosen. This represents a 24 bits instruction, which will be used in the other blocks.


IV. MUX2V4

These are simple multiplexores, used to decide which interval of the instruction needs to be used for this instance. The upper one is used for the *base register*, whilst the lower one is used for the *destination register*.

From the first table (completed in Milestone 1) we can see that the *destination registers* are either between the bits 10-7 or 3-0.

The *base registers* are either between the bits 18-15 or 14-11.

 For the first MUX, when *RegBase* is 0, the value entering through *I0* is selected, and when it is 1, the value of *I1* is selected. The output is represented by the selected value.



V. Ctrl

This block is responsible for setting the different types of signals in conformity with the *OPCODE*. The values are updated in accordance with the second table (created for Milestone 2).

Starting with the flags, we have:

- \bullet CE NF = 1 (negative flag is active)
- \bullet CE OVF = 1 (overflow flag is active)
- \bullet CE ZF = 1 (zero flag is active)
- \bullet CE CF = 1 (carry flag is active)

All of these flags are sent to ALU so that it can correctly compute the operations.

Also for ALU, we have the signal ALUOP, a 3 bits number, used to decide the current instruction.


Starting from the top towards the bottom, we have the following signals:

❖ MemWr

- > signal used in *DataMem* block to enable the memory writing (it is enabled when the signal is 1);
- > the only instruction writing in memory is MOV Wns, f.

♦ Mem2Reg

 - ➤ signal used in MUX2V16 to select whether the information is taken from the block DataMem or ALU;
- \rightarrow for 0 we read from ALU and for 1 we read from DataMem.




- **❖** RegWr
 - > signal used in the block File_Regs to enable writing in the registers (it is enabled when the signal is 1).
- **❖** Branch
 - ➤ signal used in PC_Update block in order to enable a branch jump (it is enabled when the signal is 1).
- ❖ RegBase
 - ➤ signal used in the block MUX2V4 (U_MUX_Regb) to decide which input is chosen (the bits 18-15 or 14-11 of the instruction).
- **❖** RegDest
 - ➤ signal used in the block MUX2V4 (U_MUX_Regd) to decide which input is chosen (the bits 10-7 or 3-0 of the instruction).

VI. ALU

This block is responsible for the arithmetical and logical instructions. The central elements of this block are *ALUOP* (sent from the *ctrl* block to decide which operation is performed), *RdData1* (from the base register) and *RdData2* (from the source register), which are the operands.

Then we have the *Clock* signal and the flags sent from the *ctrl* block.

 A. LSR Wb, #lit4, Wnd (Logical Right Shift by short literal). The value within the register *Wb* is right shifted by the number of bits specified by the literal value, and the result is stored in the *Wnd* register.



B. ZE Ws, Wnd (Zero extend). Zero-extends the least significant Byte from the register *Ws* and stores the result into the register *Wnd*.

 $Ws(7:0) \rightarrow Wnd(7:0)$ and

 $0 \rightarrow \text{Wnd}(15:8)$

Ex: ZE W1, W2 where (W1) = $0x1234 \Rightarrow$ (W2) $\leftarrow 0x0034$

C. BTST.Z Ws, #bit4 (Test in Ws). The number given through **#bit4** will represent the position of the bit which will be tested. Then, after testing the bit, it will be overwritten in *Z* the negated value of the tested bit.

Ex: BTST.Z W1, $0x7 \Rightarrow Z = 1$ (the seventh bit is 0)


D. INC Ws, Wd (Increment Ws). Adds 1 to the value inside the *Ws* register and stores the result inside the *Wd* register.

Ex: INC W1, W2 where (W1) = $0900 \Rightarrow$ (W2) $\leftarrow 0911$

 VII. File Regs

Inside this block we have 16 registers, noted from W0 to W15, each having a size of 16 bits. The registers are used to retain the data necessary for the operations. Thus, we write the data that has a destination register and read the data from the corresponding source register.

RdRed1 and RdReg2 represent the addresses from which we want to take the values of the operands. The actual values are sent to the RdData1 and RdData2. Likewise, WrReg holds the address at which we want to write the information, and WrData contains the actual value that we want to write.




It should be noted that the data is written only when the writing is enabled (*RegWr* is 1) and on the rising edge of the Clock signal.

 VIII. DataMem

Inside this block there is a 16x16 RAM module (16 words, each having 16 bits), and is the place where the instruction *MOV Wns, f* writes.

The input is read from the addresses 1020h (*INW0*) and 1022h (*INW1*), and the output is written at the address 1024h (*OUTW0*)




Based on the value of the *Addr*, the corresponding value inside the memory is selected and sent out through the signal *DataOut* to the *MUX2V16* block.

 IX. MUX2V16

The purpose of this MUX is to decide whether the information is read from the *DataMem* block or *ALU*, depending on the value of the signal *Mem2Reg*, sent from the *ctrl* block.

The corresponding value is then sent in the *File_Regs* block as the actual results of the operation.



Instruction coding (Milestone 1)

	 	tone 1)							
Encoding	2222 3210	1111 9876	1111 5432	11 1098	7654	321 0	Flags		
ADD	0100	Owww	wBqq	qddd	dppp	S S S	N, OV, Z, C		
SUB	0101	Owww	wBqq	qddd	dppp	SSS S	N, OV, Z, C		
AND	0110	Owww	wBqq	qddd	dppp	S S S	N, - , Z, -		
IOR	0111	Owww	wBqq	qddd	dppp	S S S	N, - , Z, -		
MOV f, wnd	1000	Offf	ffff	ffff	ffff	ddd d	none		
MOV wns,	1000	1fff	ffff	ffff	ffff	S S S	none		
BRA expr	0011	0111	nnnn	nnnn	nnnn	nnn n	none		
LSR Wb, #lit4, Wnd	1101	1110	Owww	wddd	d100	kkk k	N, -, Z, -		
ZE Ws, Wnd	1111	1011	1000	0ddd	dppp	S S	N, -, Z, C		
BTST .Z Ws, #bit4	1010	0011	bbbb	z000 0	0ppp	S S S	-, -, Z, C		
INC Ws, Wd	1110	1000	0Bqq	qddd	dppp	SSS S	DC, N, OV, Z, C		
BRA OV, Expr	0011	0000	nnnn	nnnn	nnnn	nnn n	none		
BRA C, Expr	0011	0001	nnnn	nnnn	nnnn	nnn n	none		
BRA N, Expr	0011	0011	nnnn	nnnn	nnnn	nnn n	none		
BRA Z, Expr	0011	0010	nnnn	nnnn	nnnn	nnn n	None		

Ctrl signals (Milestone 2):

Encoding	OPCODE	CE_NF	CE_OVF	CE_ZF	CE_CF	ALUOP	MemWr	Mem2Reg	RegWr	Branch	RegDest	RegBase
ADD	01000	1	1	1	1	000	X	X	1	х	1	1
SUB	01010	1	1	1	1	001	X	X	1	х	1	1
AND	01100	1	Х	1	X	010	X	X	1	х	1	1
IOR	01110	1	X	1	X	011	X	X	1	х	1	1
MOV f, wnd	10000	X	X	X	X	-	X	1	1	x	0	x
MOV wns, f	10001	X	Х	Х	X	-	1	X	Х	х	х	х
BRA expr	00110	X	Х	Х	X	-	X	X	Х	1	х	х
LSR Wb, #lit4, Wnd	11011	1	X	1	х	100	X	X	1	X	1	0
ZE Ws, Wnd	11111	1	X	1	1	101	X	X	1	х	1	х
BTST .Z Ws, #bit4	10100	x	x	1	1	110	Х	X	1	x	x	х
INC Ws, Wd	11101	1	1	1	1	111	X	X	1	х	1	Х
BRA OV, Expr	00110	X	X	х	Х	-	Х	X	X	1	х	х
BRA C, Expr	00110	X	Х	Х	Х	-	X	X	Х	1	х	X
BRA N, Expr	00110	X	X	X	Х	-	X	X	Х	1	х	х
BRA Z, Expr	00110	X	X	Х	Х	-	X	X	Х	1	х	х

